


EASTERN UNIVERSITY, SRI LANKA

FIRST EXAMINATION IN SCIENCE - 2008/2009

SECOND SEMESTER (PROPER/REPEAT)

(October/November 2010)

PH 104 AC THEORY

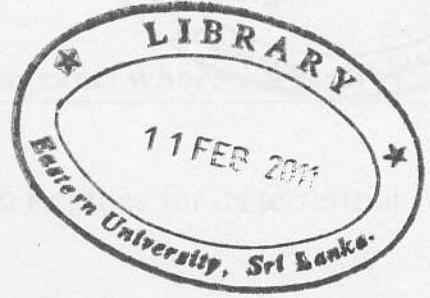

Time: 01 hour.

Answer ALL Questions


- 
1. An inductor, a capacitor and a resistor are connected in series across an *ac* power supply of voltage  $V$  and frequency  $f$ . Draw an appropriate phasor diagram for the voltage and current through each component of the circuit. State the conditions for resonance in the circuit and find an expression for the *resonance frequency* of the circuit.

A coil of resistance  $20 \Omega$  and inductance  $0.01 H$  is connected in series with a capacitance of  $4 \mu F$  across a  $100 V$ ,  $1000 Hz$  supply.

Calculate:

- (i) The circuit impedance
- (ii) The circuit current
- (iii) The phase difference between supply voltage and current

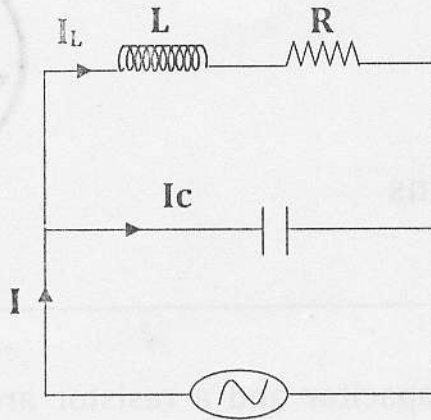2. An inductor and a resistor are connected in parallel with a capacitor as shown in the figure below. Write down the conditions for resonance in an  $LCR$  parallel circuit. Find an expression for the resonance frequency of the circuit by drawing suitable phasor diagrams.



A circuit consisting of an inductor of  $0.05\text{ H}$  and resistance  $5\ \Omega$  is in parallel with a capacitor of  $0.1\ \mu\text{F}$ . Calculate the frequency of resonance. At this frequency, find:

- (i) The impedance
- (ii) The Q-factor