

EASTERN UNIVERSITY, SRI LANKA

SECOND EXAMINATION IN SCIENCE - 2003/2004

FIRST SEMESTER

(NOV/DEC 2004)

REPEAT

PH202 - ELECTRONICS I


Time: 01 hour.

Answer ALL questions



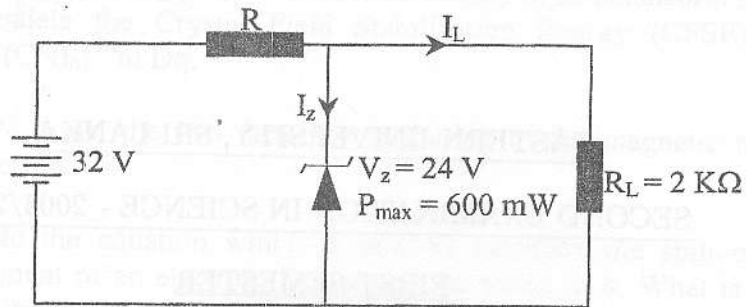1. Explain Voltage-Current characteristic of a PN – junction diode.

What do you mean by the terms Junction break down, Zener break down and Avalanche break down.



A 24 V, 600 mW Zener diode is to be used for providing a 24 V stabilized supply to a load resistance 2 K Ω as shown in the figure. If input voltage is 32 V, Calculate;


- (i) Maximum current through the Zener diode $I_{z(\text{max})}$.
- (ii) Voltage across R_L .
- (iii) Series resistance R required.
- (iv) Current across the load resistance R_L .
- (v) Total current in the circuit.
- (vi) Current across the Zener diode.

2. Describe the behavior of the NPN transistor.

Explain the function of the Emitter, Base and Collector of a transistor.

Draw and clearly label an input and an output characteristic curve of a transistor.

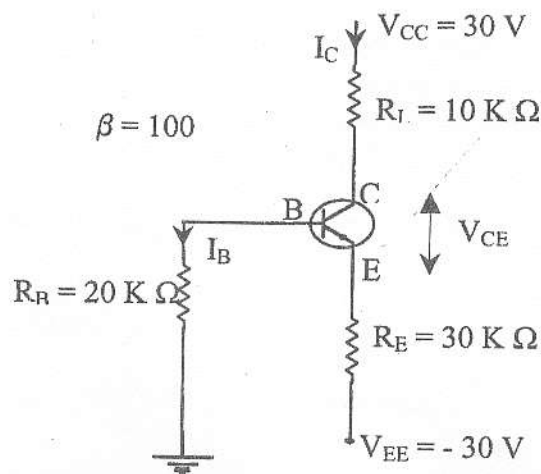What do you mean by the terms Active region, Saturation region and Cut Off region.



In the above NPN transistor circuit, assume $\beta = 100$ and V_{BE} is negligible, Find the;

- (i) I_E
- (ii) I_B
- (iii) I_C
- (iv) V_{CE}