

EASTERN UNIVERSITY, SRI LANKA

FIRST EXAMINATION IN SCIENCE - 2002/2003

(MARCH/APRIL 2004)

REPEAT

PH103 & PH104

ELECTRICITY AND MAGNETISM I AND AC THEORY

Time: 02 hour.


Answer Four questions only selecting minimum Two from each section.

---

## SECTION A

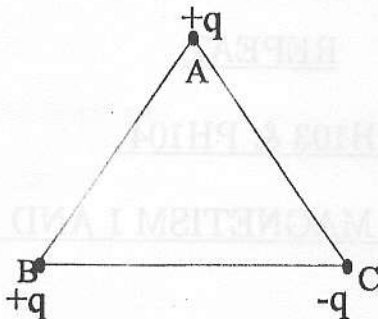1. State Coulomb's law in Electrostatics.

Three charges are arranged in an equilateral triangle as shown in the figure.



- Find the magnitude and direction of the force at point A.
- Find the magnitude and direction of the force at point C.
- If the point A is replaced by charge  $+3q$ , what is the magnitude of the force at point A?



2. State Gauss's theorem in electrostatics.

The volume charge density of a cylinder of radius  $a$  at a distance  $r$  from its axis is

$$\rho = \rho_0 \left( 1 + \frac{r^2}{a^2} \right)$$


- Show that the charge contained in the cylinder per unit length is  $\frac{3}{2}\pi\rho_0 a^2$ .
  - Find the electric field strength when  $r < a$  and  $r > a$ .
3. State Biot-Savart Law and derive an expression for the B-field produced by an infinitely long current carrying conductor at a distance  $a$ . Consider two long straight current carrying conductors carrying currents  $I_1, I_2$  in same directions as shown in the figure.

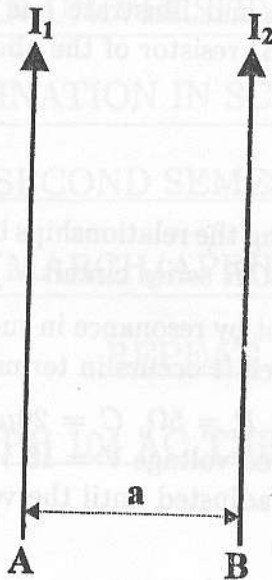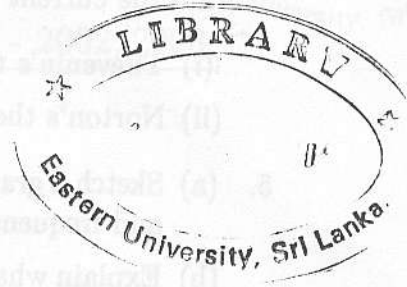- Find the magnitude and the direction of the magnetic field at the conductor B due to conductor A.



- (ii) Find the magnitude and the direction of the magnetic field at the conductor *A* due to conductor *B*.
- (iii) Find the magnitude and the direction of the force on conductor *B* due to conductor *A*.
- (iv) If  $I_1 = 10A$ ,  $I_2 = 8A$  and  $a = 4cm$  calculate the magnetic force on conductor *B* due to conductor *A*. Assume that  $\mu_0 = 4\pi \times 10^{-7}Hm^{-1}$ .

SECTION B

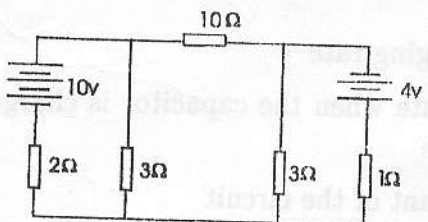

4. State Thevenin's theorem and illustrate one of it with an example. Find the current in the  $10\Omega$  resistor of the above circuit using
- Thevenin's theorem
  - Norton's theorem
5. (a) Sketch a graph showing the relationships between current, impedance and frequency in a  $LCR$  series circuit.
- (b) Explain what is meant by resonance in such a circuit and calculate the frequency at which it occurs in terms of  $L$  and  $C$ .
- (c) A series circuit with  $R = 5\Omega$ ,  $C = 20\mu F$  and a variable inductance  $L$  has an applied voltage  $V = 10 \text{ Volts}$  with a frequency of  $1000 \text{ radsec}^{-1}$ .  $L$  is adjusted until the voltage across the resistor is a minimum. Find
- inductance of the inductor
  - the current through the circuit
  - the voltage across the capacitor
  - the voltage across the resistor
6. A series circuit consists of a capacitor  $C$ , resistor  $R$  and a battery of e.m.f  $E$ . The capacitor is initially uncharged. Show that after a time  $t$  the capacitor carries a charge  $Q$  given by

$$Q = Q_0 \left[ 1 - \exp\left(-\frac{t}{CR}\right) \right]$$

where  $Q_0$  is the final charge on the capacitor.

A  $20\mu F$  capacitor is connected in series with a  $1M\Omega$  resistor and a  $100V$  battery. Calculate

- the initial charging rate
- the charging rate when the capacitor is charged to one-fourth of the final charge
- the time constant of the circuit