



EASTERN UNIVERSITY, SRI LANKA

THIRD EXAMINATION IN SCIENCE - 2003/2004

FIRST SEMESTER

(NOV/DEC 2004)

REPEAT

PH301 - ELECTRONICS II

Time: 01 hour.

Answer ALL questions

$$4x + 3y = 12$$
$$2x + 5y = 10$$

2. Draw the symbols and truth table for the following

- (a) AND
- (b) NAND
- (c) OR
- (d) NOR

Simplify the following expressions.

- (i) $Z = (A+B)(A-B)$
- (ii) $Z = (A+B)(A+B+D)$
- (iii) $Z = \overline{A}BCD + A\overline{B}CD + ABC\overline{D} + ABCD$
- (iv) $Z = \overline{A}C(\overline{A}BD + ABCD) + ABC$
- (v) $Z = (A+B)(A+C)(B+C)$

A lamp in a room is to be operated from two switches, one at the back door and one at the front door. The lamp is to be ON if the front switch is ON and the back switch is OFF or if the front switch is OFF and the back switch is ON. The lamp is to be OFF if both switches are OFF or if both switches are ON. Let a HIGH (1) output represent the ON condition and a LOW (0) output represent the OFF condition. Construct a logic circuit for this system.


1.

(i) Describe the major properties of an ideal operational amplifier.

Draw circuits and derive the relation between the input and output signals of the following operational amplifier.

- (a) Inverting amplifier
- (b) Non-Inverting amplifier
- (c) Adder

(ii)

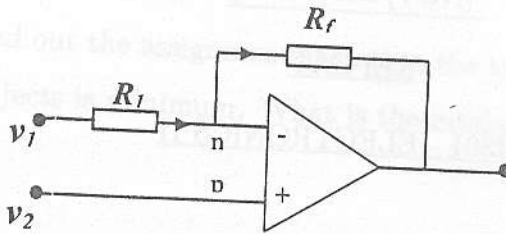

In the above circuit if $R_i = 1 \text{ K}\Omega$, $R_f = 10 \text{ K}\Omega$, $v_1 = 4 \text{ V}$ and $v_2 = 4.5 \text{ V}$ then determine the output voltage and CMRR of the differential amplifier.

(iii) Solve the following simultaneous equations for x and y using operational amplifier.

$$a_1x + b_1y = c_1$$

$$a_2x + b_2y = c_2$$

2. Draw the symbols and truth table for the following

(a) AND

(b) NAND

(c) OR

(d) NOR

Simplify the following expressions.

(i) $Z = (\overline{A+B}) (A+B)$

(ii) $Z = (\overline{A+B}) (A+B+D) \overline{D}$

(iii) $Z = \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D}$

(iv) $Z = \overline{A}C(\overline{A+B}) + \overline{A}B\overline{C}\overline{D} + A\overline{B}C$

(v) $Z = (A+B) (\overline{A+C})(\overline{B+C})$

A lamp in a room is to be operated from two switches, one at the back door and one at the front door. The lamp is to be ON if the front switch is ON and the back switch is OFF, or if the front switch is OFF and the back switch is ON. The lamp is to be OFF if both switches are OFF or if both are ON. Let a HIGH (1) output represent the ON condition and a LOW (0) output represent the OFF condition. Construct a logic circuit for this system.